

Lab 05: The Awesome Vending Machine

Submission deadlines:

Source Code:	2019/10/29 18:30
Report:	2019/11/03 23:59

Objective

- To be familiar with modeling finite state machines with Verilog.
- To be familiar with the FPGA design flow, the demo-board I/Os

Description

Design a controller for the Awesome Vending Machine which is very similar to an actual vending machine. It behaves as follows:

- The basic concept of how this vending machine works:
 - Initially, the machine will show “0000” on the 7-segment display. All LEDs will be turned off.
 - When the customer presses the money button, the corresponding coin will be deposited into the machine. The two **rightmost** 7-segment digits will show the balance (the amount of deposited money). If the balance is more than the price of the drinks, the corresponding LEDs will light up.
 - When the customer presses the cancel button, the machine will return the deposited money.
 - When the customer presses the drink button **once**, the two **leftmost** 7-segment digits will show the price of the corresponding drink. When the customer presses the same drink button **again**, the drink will come out if the deposited money is enough.
 - When dropping the drink, the 7-segment display will show its name. And all LEDs should be turned off.
 - When the drink has been dropped, the change should be returned. The 7-segment display will show the decreasing balance and return the change coin by coin with corresponding LEDs lighting up.
- The detailed spec:
 - INITIAL state: After being reset, the machine goes to the

INITIAL state. The 7-segment display will show “0000”. There are LEDs corresponding to *enough_A*, *enough_B*, and *drop_money*(10 LEDs). All the LEDs will be off initially. Then, the machine goes to the DEPOSIT state.

■ DEPOSIT state:

- ◆ First, the customer may deposit \$5 coin by pressing the *money_5* button or \$10 by pressing the *money_10* button. Every time after the customer deposits a coin (\$10 or \$5), the two **rightmost** 7-segment digits will show the total amount of money that has been deposited so far (*balance*). The price of the two drinks: *drink_A* and *drink_B* are *price_A* = \$20 and *price_B* = \$25, respectively. The machine will return the deposited money if the customer presses the *cancel* button. The *balance* cannot be over 99. The LED *enough_A* or *enough_B* will light up if the *balance* is more than the price of *drink_A* or *drink_B*, respectively.
- ◆ If the customer presses *drink_A* or *drink_B* **once**, the two **leftmost** 7-segment digits (*price*) will show the *price_A* or *price_B*. If the customer presses *drink_A* first and then presses *drink_B*, the price will be *price_B*, vice versa.
- ◆ If the customer presses the same drink button twice, the machine will enter the BUY state if the *balance* is enough.

■ BUY state:

- ◆ The LED *enough_A* and *enough_B* would be turned off.
- ◆ The 7-segment display shows the name of the selected drink for one clock cycle (**with the frequency of $\text{clk}/(2^{26})$**). The names of *drink_A* and *drink_B* can be defined freely. But limited to 4 characters. You can refer to the following graph.



- **CHANGE state:** The two rightmost 7-segment digits will show the change to be returned to the customer (*balance – price*). If there are more than or equal to \$10 to return, the change will be decreased by \$10 (to simulate dropping a coin of \$10), and the ten leftmost LEDs corresponding to the *drop_money* (LD15~LD6) will light up at each clock cycle (**with the frequency of $\text{clk}/(2^{26})$**) until the two rightmost 7-segment digits show "00" or "05". If there is less than \$10 to be returned, the change will be decreased by \$5 once and the five leftmost LEDs corresponding to the *drop_money* (LD15~LD11) will light up for one clock cycle (**with the frequency of $\text{clk}/(2^{26})$**).
- ***Bonus:** In the DEPOSIT mode, if the customer doesn't take any action for about 5~10 seconds (see Hint c), the leftmost 7-segment will show "00", and the machine will return the change the customer has deposited.

I/O signal specification:

- **clk:** clock signal with the frequency of 100MHz (connected to pin W5).
- **rst:** active-high reset (connected to SW0).
- ✧ Each signal from the pushbutton in the following have to be processed by a debouncer, and then a one_pulse circuit.
 - ◆ **money_5:** deposit a \$5 coin (connected to BTND).
 - ◆ **money_10:** deposit a \$10 coin (connected to BTNU).
 - ◆ **cancel:** cancel current drink choice and return the *balance* if

there is any. (connected to **BTNC**).

- ◆ **drink_A**: show *price_A* or confirm the purchase of *drink_A* (connected to **BTNL**).
- ◆ **drink_B**: show *price_B* or confirm the purchase of *drink_B* (connected to **BTNR**).
- **enough_A**: indicating if the *balance* is more than the *price_A* (connected to **LD1**).
- **enough_B**: indicating the *balance* is more than the *price_B* (connected to **LD0**).
- **drop_money[9:0]**: the drop_money signal (connected to **LD15 ~ LD6**).
- **DIGIT[3:0]**: signals to enable one of the 7-segment digits.
- **DISPLAY[6:0]**: signals to show the digits on the 7-segment display.

Note:

1. All the signals of the pushbutton should be properly processed with the debounce and one pulse.
2. The clock frequency of each debouncer or one-pulse circuit is $\text{clk}/(2^{16})$
3. The clock frequency of the seven-segment display controller is $\text{clk}/(2^{13})$
4. Demo video:

<https://www.youtube.com/watch?v=UO2x2e1i4js&feature=youtu.be>

Hint:

1. You must design at least one finite state machine (FSM).
 - a) There should be at least four states. Think carefully for the operation frequencies of the pushbuttons and 7-segment display.
 - b) The proper duration for each state may be:
 1. INITIAL: $\text{clk}/2^{16}$
 2. DEPOSIT: $\text{clk}/2^{16}$
 3. BUY: $\text{clk}/2^{26}$
 4. CHANGE: $\text{clk}/2^{26}$

You may operate at a higher clock rate and use a counter to slow down the display rate (e.g., the FSM can operate at the

clock rate of $\text{clk}/2^{16}$. But every time when it enters the BUY or CHANGE state, it will stay for at least 2^{10} cycles before changing to other states). Or you may use a clock selector as a quick fix.

- c) $\text{clk}/2^{29}$ is about 5 seconds. You may design a counter to measure this period for the bonus.

2. You can use the following template for your design.

```
module lab05(clk, rst, money_5, money_10, cancel, drink_A,
drink_B, drop_money, enough_A, enough_B, DIGIT, DISPLAY);
    input clk;
    input rst;
    input money_5;
    input money_10;
    input cancel;
    input drink_A;
    input drink_B;
    output reg[9:0] drop_money;
    output reg enough_A;
    output reg enough_B;
    output [3:0] DIGIT;
    output [6:0] DISPLAY;
    //add you design here
endmodule
```

Attention:

1. You should hand in only one Verilog file, **lab05.v**. If you have several modules in your design, integrate them in lab05.v. **(Please do not hand in any compressed files, which will be considered as an incorrect format.)**
2. You should also hand in your report as lab05_report_StudentID.pdf (i.e., lab05_report_1070666666.pdf).
3. You should be able to answer questions of this lab from TA during the demo.
4. You need to generate bitstream before demo.